

ContainerPower Energy Solutions

Pure sine wave inverter module



Overview

To set up the automatic voltage correction circuit, feed a stable 230V or 110V as per your inverter specs to the input side of the circuit. Next, adjust the 10k preset carefully such that the red LEDs just light up. That's all, seal the preset and connect it. To set up the automatic voltage correction circuit, feed a stable 230V or 110V as per your inverter specs to the input side of the circuit. Next, adjust the 10k preset carefully such that the red LEDs just light up. That's all, seal the preset and connect the circuit with the above Arduino board for implementing the intended automatic output voltage.

To ensure that the mosfet stages initiate with a delay during the Arduino booting or start up, you may modify left side BC547 transistors into delay ON stages, as shown below. This will safeguard the mosfets and prevent them from burning during power switch ON Arduino booting.

If you are not comfortable with the response of the above passive delay ON timer circuit, you can employ the following configuration using BJTs and a relay. This design is extremely reliable and will effectively protect your Arduino and the inverter from burning due to a malfunctioning delay effect. Just add this to the above inverter configuration.

Just like any other inverter the output from this design can rise to unsafe limits when the battery is fully charged. To control this an automatic voltage regulator could be employed as shown below. The BC547 collectors should be connected to the bases of the left side BC547 pair, which are connected to the Arduino via 10K resistors. For an isolated.

The complete diagram using the automatic voltage regulator and the delay ON timer would look like this:

Pure sine wave inverter module

Contact Us

For catalog requests, pricing, or partnerships, please visit:
<https://www.websparafotografos.es>